

নথমো

১৯৮২ সালের নথমো. মুক্তিপ্রস্তুতি।

১

১৯৮২ ১ ২৫৮.

১ ম R_T ক'প আ-১

$$R_{T1} = 2 + 2.5 = 4.5 \Omega$$

$$R_{T2} = 7 + 5 = 12 \Omega$$

$$R_{T3} = R_{T1} // R_{T2} = \frac{4.5 \times 12}{4.5 + 12} = \frac{54}{16.5} = 3.272 \Omega$$

$$R_{T4} = R_{T3} // 12 \Omega = \frac{\frac{54}{16.5} \times 12}{\frac{54}{16.5} + 12} = \frac{3.272 \times 12}{3.272 + 12} = \frac{39.264}{15.272} = 2.591 \Omega$$

$$R_{T5} = 9 \Omega // R_{T4} = \frac{9 \times 2.591}{9 + 2.591} = \frac{23.319}{11.591} = 2.026 \Omega$$

$$R_{T6} = R_{T5} + 2 + 2 = 2.026 + 4 = 6.026 \Omega$$

$$R_{T7} = 6 // 6 // R_{T6} = 6 // 6 // 6 = 2 \Omega$$

$$R_{T8} = 2 \Omega + 7 \Omega = 9 \Omega$$

$$R_{T9} = 9 \Omega // R_{T8} = \frac{9 \times 9}{9 + 9} = 4.5 \Omega$$

$$R_{T10} = 4.5 + 2.5 = 7 \Omega$$

$$R_{T11} = 7 \Omega // 5 \Omega = \frac{7 \times 5}{7 + 5} = 2.916 \Omega$$

$$R_T = 2.916 + 1 + 12 = 15.916 \Omega - 12 \Omega = 3.916 \Omega$$

② In R_T s. umfang A-D

$$R_{T_1} = 10 // 10 = 5 \Omega$$

$$R_{T_2} = 10 // 10 = 5 \Omega$$

$$R_{T_3} = R_{T_1} + R_{T_2} = 5 + 5 = 10 \Omega$$

$$R_{T_4} = 10 // 10 = 5 \Omega$$

$$R_{T_5} = 10 // 10 = 5 \Omega$$

$$R_{T_6} = R_{T_4} + R_{T_5} = 5 + 5 = 10 \Omega$$

$$R_{T_7} = R_{T_3} // R_{T_6} = 10 // 10 = 5 \Omega$$

$$R_{T_7} = 5 \Omega$$

$$R_{T_9} = R_{A-D} = 5 \Omega \quad \text{---} \quad \text{D}$$

(1) in $\$_1$, $\$_1$, $\$_2$

$$R_{T1} = 1.5 // 3 \Omega = 1 \Omega$$


$$R_{T2} = 1 + 2.8 + 1 = 4.8 \Omega$$

$$R_{T3} = 7.5 // R_{T2} = \frac{7.5 \times 4.8}{7.5 + 4.8} = 2.926 \Omega$$

$$R_{T4} = R_{T3} // 5 \Omega = \frac{2.926 \times 5}{2.926 + 5} = 1.8463 \Omega$$

$$R_{T5} = R_{T4} // 8 \Omega = \frac{1.846 \times 8}{1.846 + 8} = 1.5 \Omega$$

$$R_T = 0.5 + 1.5 + 1 = 3 \Omega$$
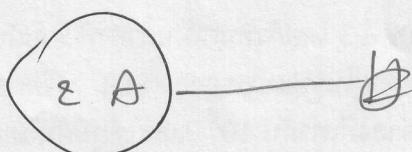
$$I_T = \frac{E}{R_T} = \frac{6}{3} = 2 A$$


$$V_{R8\Omega} = E - I_T \times 0.5 - I_T \times 1$$

$$V_{R4\Omega} = 6 - (2 \times 0.5 + 2 \times 1) = 6 - 3 = 3 V$$

$$V_{R5\Omega} = V_{R4\Omega} = 3 V$$

$$I_1 = \frac{3 V}{5 \Omega} = 0.6 A$$


$$45^\circ \quad I_0 = \frac{I_T \times 8}{8 + R_{T4}} \quad \cancel{\text{I}_{T4}}$$

$$I_0 = \frac{2 \times 8}{8 + 1.8463} = 1.6249 \text{ A}$$

$$I_1 = \frac{I_0 \times R_{T2}}{5 + R_{T3}} = \frac{1.6249 \times 2.926}{5 + 2.926} \text{ A}$$

$$I_1 = 0.599 \approx 0.6 \text{ A} \quad \cancel{\text{A}}$$

$$V_{R_5} = V_{T8} = V_{T9.5} = I \times$$

$$I_{R_{9.5}} = \frac{3}{7.5} = 0.4 \text{ A}$$

$$I_{T9.5} = \frac{3}{4.8} = \frac{3}{4.8} \text{ A} \doteq 0.625 \text{ A}$$

$$I_2 = \frac{I_{T9.5} \times 1.5}{3 + 1.5} = \frac{0.625 \times 1.5}{3 + 1.5}$$


$$\Phi_2 = 0.208 \text{ A} \quad \cancel{\text{A}}$$

④

④

20mΩ
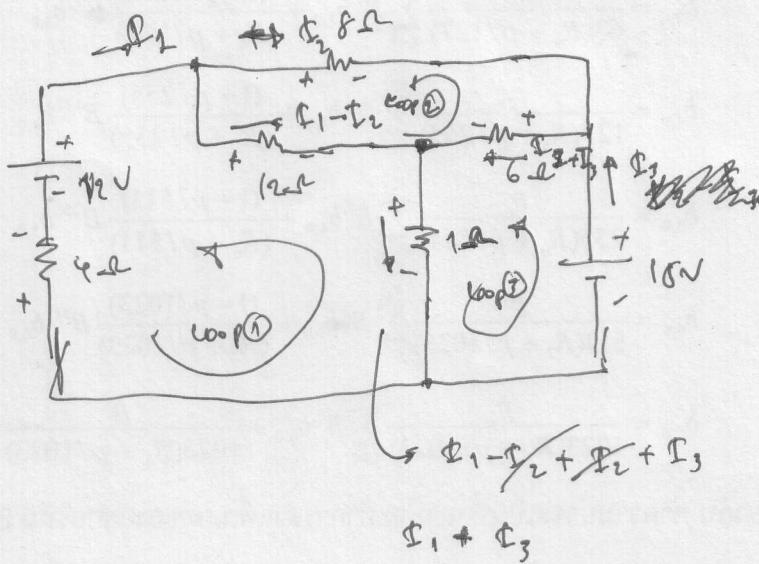
$$\frac{0.1 \text{ A}}{20 \text{ m}\Omega} = 0.05 \text{ A}$$



Loop ①

KVL

$$+ 4I_1 - 12 + 12(I_1 - I_2) + 1(I_1 + I_3) = 0$$

$$4I_1 - 12 + 12I_1 - 12I_2 + I_1 + I_3 = 0$$

$$17I_1 - 12I_2 + I_3 = 12 \quad \text{--- } ①$$

Loop ②

$$+ 12(I_1 - I_2) - 6(I_3 + I_2) - 8I_2 = 0$$

$$12I_1 - 12I_2 - 6I_3 - 6I_2 - 8I_2 = 0$$

$$12I_1 - 26I_2 - 6I_3 = 0 \quad \text{--- } ②$$


Loop ③

$$-15 + 6(I_2 + I_3) + 1(I_1 + I_2) = 0$$

$$-15 + 6I_2 + 6I_3 + I_1 + I_2 = 0$$

$$I_1 + 6I_2 + 7I_3 = 15 \quad \text{--- } ③$$


(b)

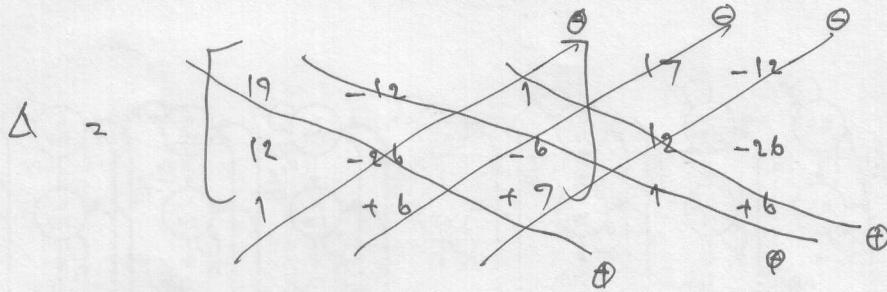

$$= -3044 + 72 + 72 + 26 + 612 + 1008$$

$$\Delta = \cancel{1304} - 1304$$

$$\Phi = \Sigma_2 =$$

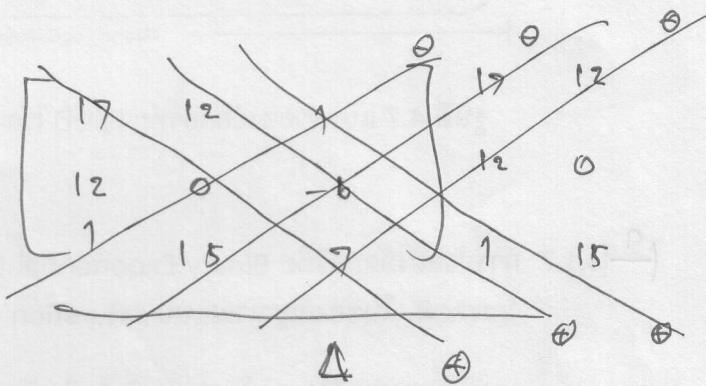


$$\Phi = \frac{0 - 72 + 180 - 0 + 1530 - 1008}{-1304}$$

$$\Phi = \frac{630}{-1304} = -0.483 \text{ A} \quad \text{Anfangsspannung}$$

⑦

⑤ ~~15 mesh~~
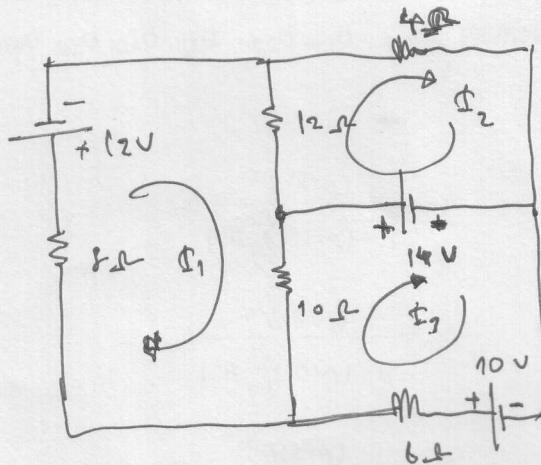
$$\begin{aligned} \Phi_2 &= 0.148 \text{ A} & \text{wtr } R_{10\Omega} \\ \Phi_3 &= 0.942 \text{ A} & \text{wtr } R_{12\Omega} \\ V_x &= 9.83 \text{ V} & \text{wtr } R_{12\Omega} \end{aligned}$$



loop Φ_1

$$(8 + 10 + 12)\Phi_1 - 12\Phi_2 - 10\Phi_3 = -12$$

$$30\Phi_1 - 12\Phi_2 - 10\Phi_3 = -12 \quad \text{--- } ①$$

loop Φ_2 * $16\Phi_2 - 12\Phi_1 = 14$

$$-12\Phi_1 + 16\Phi_2 = 14 \quad \text{--- } ②$$


loop Φ_3

$$16\Phi_3 - 10\Phi_1 = -14 + 10$$


$$-10\Phi_1 + 16\Phi_3 = -4 \quad \text{--- } ③$$

Δ =
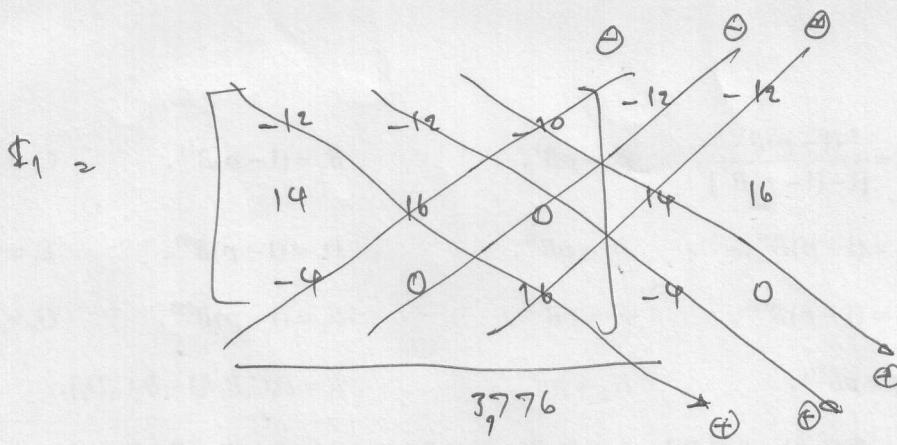
$$\begin{matrix} 30 & -12 & -10 & 30 & -12 \\ -12 & 16 & 0 & -12 & 16 \\ -10 & 0 & 16 & -10 & 0 \\ 30 & -12 & -10 & 30 & -12 \\ -12 & 16 & 0 & -12 & 16 \end{matrix} \equiv 7680 - 1600 - 2304 = 3776$$


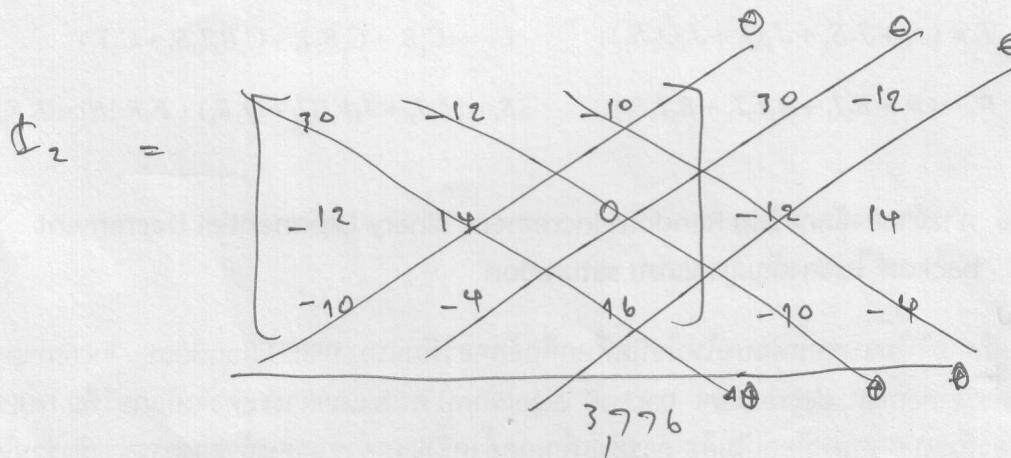
$$I_1 = \frac{-3072 + 0 + 0 - 640 - 0 + 2688}{3776} = \frac{-1028}{3776} = -0.2711 \text{ A}$$



$$I_2 = \frac{+6720 + 0 - 480 - 1400 - 0 - 2304}{3776} = \frac{2576}{3776}$$


~~\$I_2 = 0.671\$~~

$$I_2 = 0.671 \text{ A}$$

Then we have to find \$I_1\$ from the nodal

$$\text{currents in } R_{12} \text{ is } I_1 + I_2 = 0.2711 + 0.671$$

I_1 with R_{12} is 0.9429 A

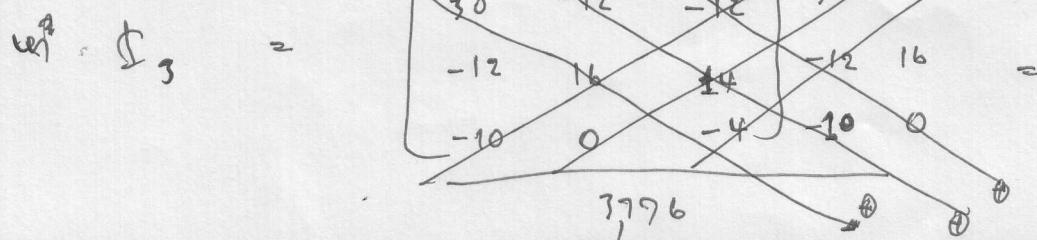


$$\Phi_3 = \frac{-1920 + 1680 + 0 - 1920 - 0 + 576}{3776} = -\frac{1584}{3776}$$

$$\Phi_3 = -0.419 \quad \text{number } \Phi_3 \text{ turns per rev}$$

$$\therefore \Phi_{R_{10A}} = \cancel{\Phi_{R_3}} \quad \Phi_3 - \Phi_1 = 0.419 - 0.2911 \quad A$$

$$\boxed{\Phi_{R_{10A}} = 0.148 \text{ A}} \quad \cancel{A}$$

~~if~~ V_x

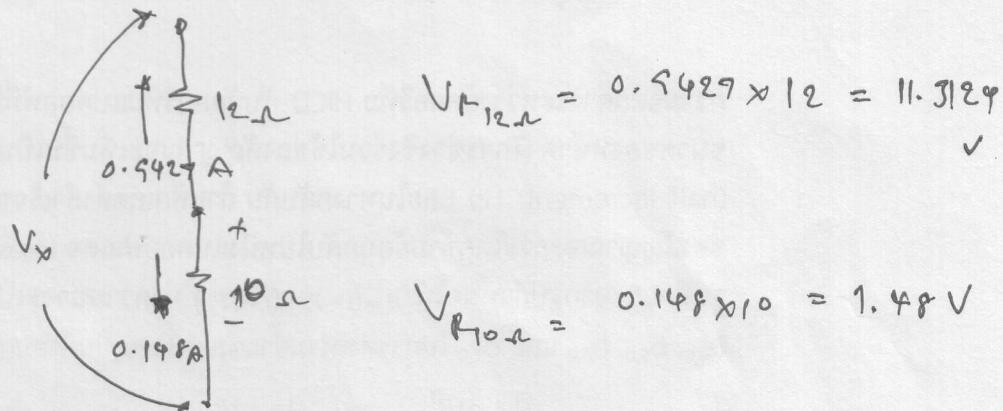

$$V_x = V_{R_{12A}} - V_{R_{10A}} = 11.3124 - 1.48$$

$$\boxed{V_x = 9.83 \text{ V}} \quad \cancel{A}$$

(b) Find node voltage at Φ_1, Φ_2, Φ_3

$$\text{At } \Phi_{100} \quad I_1 = 1 \text{ A}$$

~~$I_2 = 0.5 \text{ A}$~~

~~$I_3 = 0.5 \text{ A}$~~

Now

$$V_A = 6 \text{ V} \rightarrow \text{Supply voltage}$$

Node A \Rightarrow

$$I_5 = I_1 + I_3 \quad \dots \quad ①$$

$$I_1 = \frac{V_A - (-6)}{12} = \frac{V_A + 6}{12}$$

$$I_1 = \frac{6+6}{12} = \frac{12}{12} = 1 \text{ A} \quad \text{Ans}$$

Node B

$$I_3 + I_2 = I_4$$

$$\frac{V_B - V_A}{2} + \frac{0 - (-6) - V_B}{4} = \frac{(V_B - 1)}{4}$$

$$\frac{6 - V_B}{1} + \frac{b}{4} = \frac{V_B - 1}{4} = \frac{V_B}{4} - \frac{1}{4}$$

$$\frac{b - V_B}{4} + 0.75 = \frac{V_B}{4} - \frac{1}{4}$$

$$b + 0.75 + 0.25 = \cancel{0.25 V_B} + \cancel{V_B}$$

$$b = (0.25 + 1)V_B = 1.25V_B$$

Node B

(11)

$$I_3 + I_2 = I_4$$

$$\frac{V_A - V_B}{2} + \frac{6 - V_B}{8} = \frac{V_B - 1}{4}$$

$$\frac{V_A}{2} - \frac{V_B}{2} + \frac{6}{8} - \frac{V_B}{8} = \frac{V_B}{4} - \frac{1}{4}$$

~~$$0.5V_A - 0.5V_B + 0.75 - 0.75V_B = 0.25V_B - 0.25$$~~

$$V_A = 6V$$

$$0.5(6) + 0.75 + 0.25 = 0.5V_B + 0.75V_B + 0.25V_B$$

$$4 = 1.5V_B$$

$$V_B = \frac{4}{1.5} = 2.666V$$


$$I_2 = \frac{6 - V_B}{8} = \frac{6 - 2.666}{8} = \underline{0.416} A$$

$$I_3 = \frac{V_A - V_B}{2} = \frac{6 - 2.666}{2} = \underline{1.667} A$$

$$V = 3 \text{ V. (Kontinu)} \quad (12)$$

(7) $\text{ven } V.$

(Number) V_1

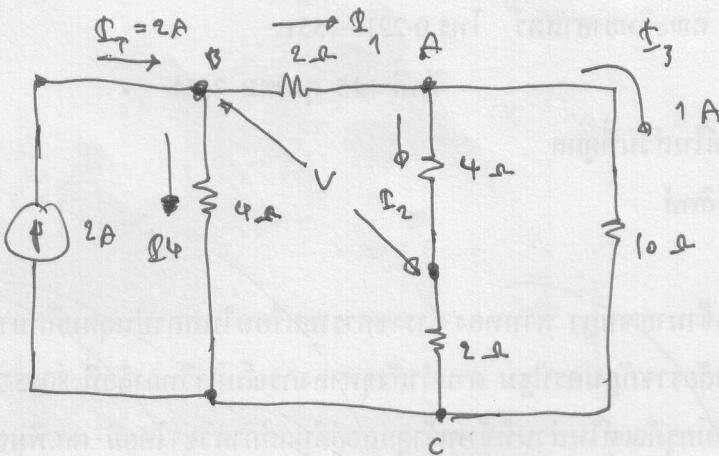

$$\text{Durchfluss } I_3 = 1 \text{ A}$$

$$V_{R_{10}} = 1 \times 10 = 10 \text{ V}$$

$$I_2 = \frac{V_{R_{10}}}{6} = \frac{10}{6} = 1.666 \text{ A}$$

$$I_1 = I_2 + I_3 = 1 + 1.666 = 2.666 \text{ A}$$

$$V_{R_2 \text{ m}} = R_2 I_1 \times 2 \Omega = 2.666 \times 2 = 5.333 \text{ V.}$$


$$V_{R_4 \text{ m}} = V_{R_2 \text{ m}} + V_{A_C} = 5.333 + 10$$

$$V_{R_4 \text{ m}} = 15.333 \text{ V} = V_{B_C}$$

$$I_4 = \frac{V_{R_4 \text{ m}}}{4 \Omega} = \frac{15.333 \text{ V}}{4} = 3.8333 \text{ A}$$

$$I_T = I_4 + I_1 = 2.666 + 3.8333 = 6.499 \text{ A}$$

1600 Suez Rd Davao

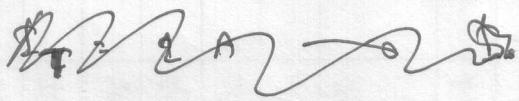25 

$$\Phi_T = \frac{2 \times 1}{6.499} A \rightarrow \Phi_L = 1 A$$

$$\Phi_T = 2 A \rightarrow \Phi_L = 2$$

$$\Phi_L = \frac{2 \times 1}{6.499} = 0.3079 A$$

$$\therefore \Phi_2 \text{ rev} = \frac{1.666}{6.499} = 0.25634 A$$

$$\Phi_1 \text{ rev} = \frac{2.666}{6.499} = 0.4102 A$$

V = 1150 turns around $R_{2,2}$ and $R_{4,2}$

$$V_{R_{2,2}} = \Phi_1 \times 2 \pi = 0.4102 \times 2 = 0.820 V$$

$$V_{R_{4,2}} = \Phi_2 \times 4 \pi = 0.25634 \times 4 \pi = 1.028$$


$$V = V_{R_2} + V_{R_4} = 0.82 + 1.028$$

$$V = 1.845 V$$

$$V = 3.636 \text{ V}$$

⑧ If superposition method.

19

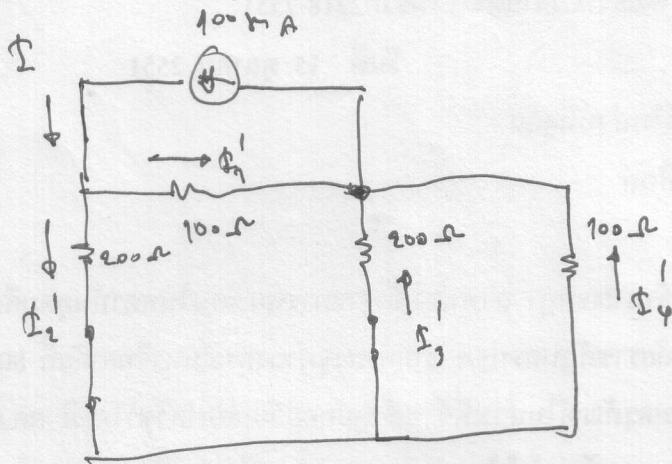

$$R_{T_1} = 200 // 400 = 66.66 \Omega$$

$$R_{T_2} = 200 + R_{T_1} = 200 + 66.66 = 266.66 \Omega$$

$$I_1' = \cancel{200} \frac{I \times R_{T_2}}{100 + R_{T_2}} = \frac{200 \text{ mA} \times 266.66}{100 + 266.66}$$


$$I_1' = 72.726 \text{ mA}$$

$$I_2' = I - I_1' = 100 - 72.726 = 27.273 \text{ mA}$$

$$I_2' = \frac{I \times 100}{266.66 + 100} = \frac{100 \text{ mA} \times 100}{366.66} = 27.273 \text{ mA}$$

$$I_3' = \frac{I_2' \times 100}{200 + 100} = \frac{27.273 \times 100}{300} = 9.091 \text{ mA}$$
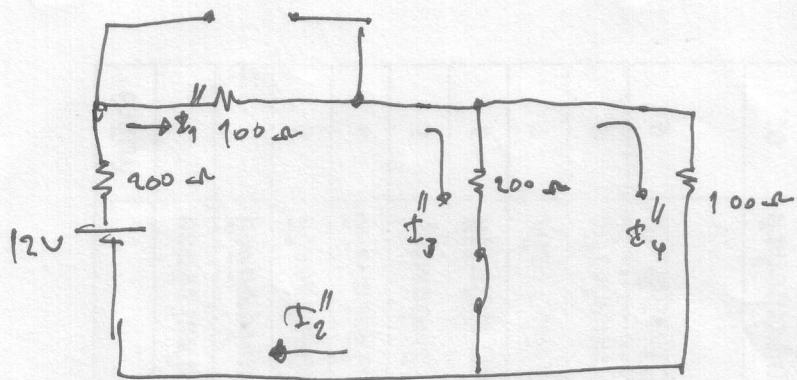
$$I_4' = I_2' - I_3' = 27.273 - 9.091 = 18.1819 \text{ mA}$$



$$I_1'' = I_2''$$

$$R_{T1} = \frac{200 \times 100}{200 + 100} = 66.66 \text{ ohm}$$


$$I_1'' = I_2'' = \frac{12}{100 + 100 + 66.66} = 0.032797 \text{ A}$$

$$I_1'' = I_2'' = 32.7278 \text{ mA}$$

$$I_3'' = \frac{I_1'' \times 100}{200 + 100} = \frac{32.7278 \times 100}{300} = 10.909 \text{ mA}$$

$$I_4'' = I_1'' - I_3'' = 32.7278 - 10.909 = 21.8185 \text{ mA}$$

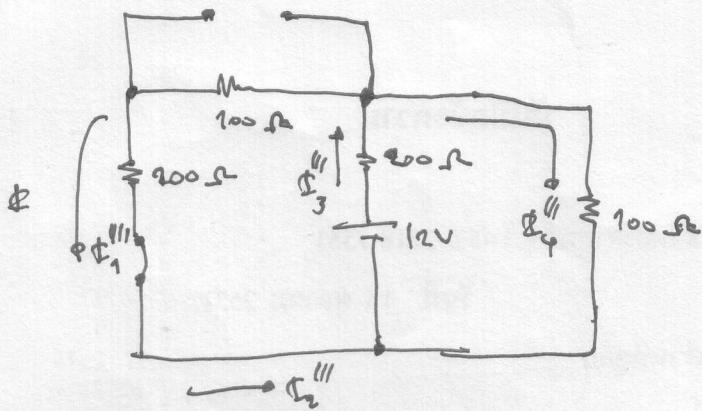~~$$I_4'' = \frac{I_1'' \times 200}{300} = 21.8185 \text{ mA}$$~~



$$\boxed{V = \mathfrak{I}_q \times 100 \Omega}$$

$$V = 21.6165 \times 100$$

$$V = 2.165 V \rightarrow b$$

$$I_1''' = I_2'''$$

$$R_{T_1} = 200 + 100 = 300 \Omega$$

$$R_{T_2} = R_{T_1} // 100 = \frac{300 \times 100}{300 + 100} = 90 \Omega$$

$$R_T = 200 + R_{T_2} = 290 \Omega$$

$$I_3''' = \frac{12}{290} = 43.676 \text{ mA}$$

$$I_1''' = I_2''' = \frac{I_3''' \times 100}{300 + 100} = \frac{43.676 \times 100}{\cancel{400}} = 10.905 \text{ mA}$$

$$I_4''' = I_3''' - I_1''' = 43.676 - 10.905 = 32.771 \text{ mA}$$

$$I_4''' = I_3''' - I_1''' = 43.676 - 10.905 = 32.771 \text{ mA}$$




$$I_4''' = \frac{I_3''' \times 300}{400} = \frac{43.676 \times 300}{400} = 32.771 \text{ mA} \rightarrow b$$

$$I_4''' = I_4''' + I_4'' - I_4' = 32.771 + 21.8185 - 32.771 \text{ mA}$$

$$I_4''' = 21.8185 \text{ mA}$$

(17)

(8)

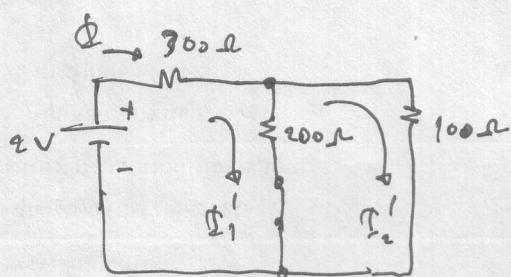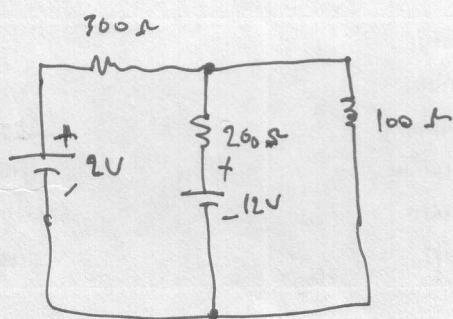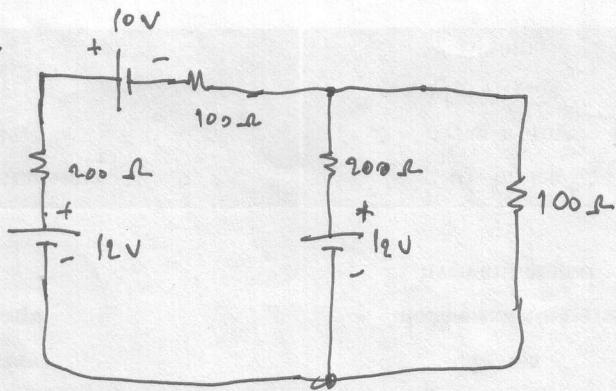


$$R_{T_1} = \frac{200 \times 100}{300} = 66.66 \Omega$$

$$R_T = 300 + 66.66 = 366.66 \Omega$$

$$\Phi = \frac{2V}{R_T} = \frac{2}{366.66} = 5.454 \text{ mA}$$
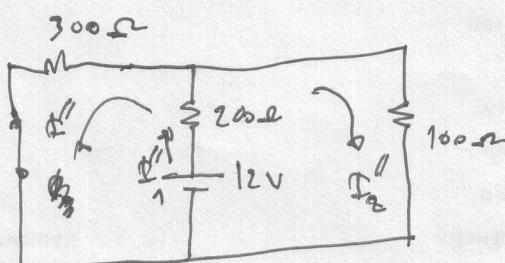
$$I_2' = \frac{\Phi \times 200}{200 + 100} = \frac{5.454 \times 200}{300} = 3.636 \text{ mA}$$



$$R_T = (300 // 100) + 200$$

$$= 75 + 200 = 275 \Omega$$

$$I_1' = \frac{12}{275} = 0.43636 \text{ mA}$$

$$\Phi_2'' = \frac{\Phi_1'' \times 300}{400} = \frac{43.636 \times 300}{400}$$

$$= 32.727 \text{ mA}$$

$$\Phi_2 = \Phi_1' + \Phi_2'' = 3.636 + 32.727 = 36.363 \text{ mA}$$

$$V = I_a \times 100 = 36.363 \text{ mA} \times 100 =$$





$$V = 3.636 \text{ } V \rightarrow A$$

(5)

in Φ_x für Trennung von Säulen

$$R_x = 2.609 \text{ m}\Omega$$

(6)

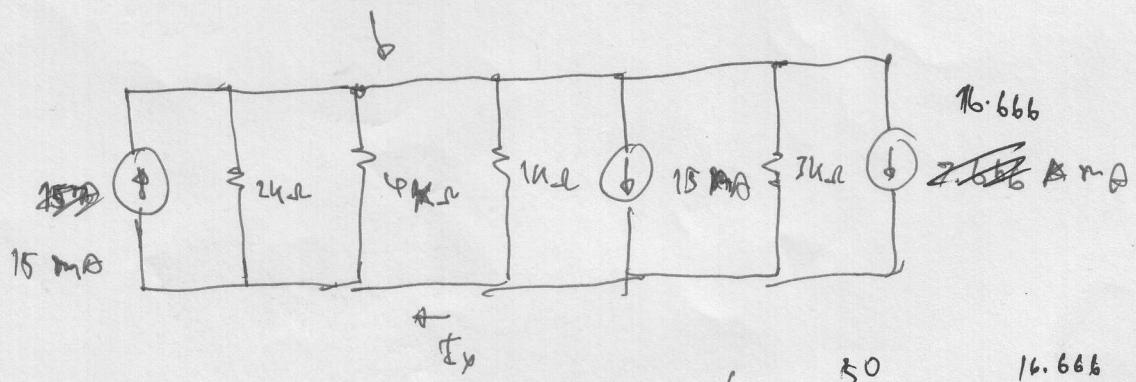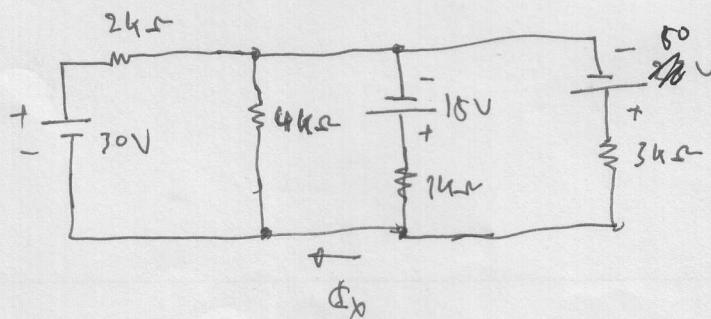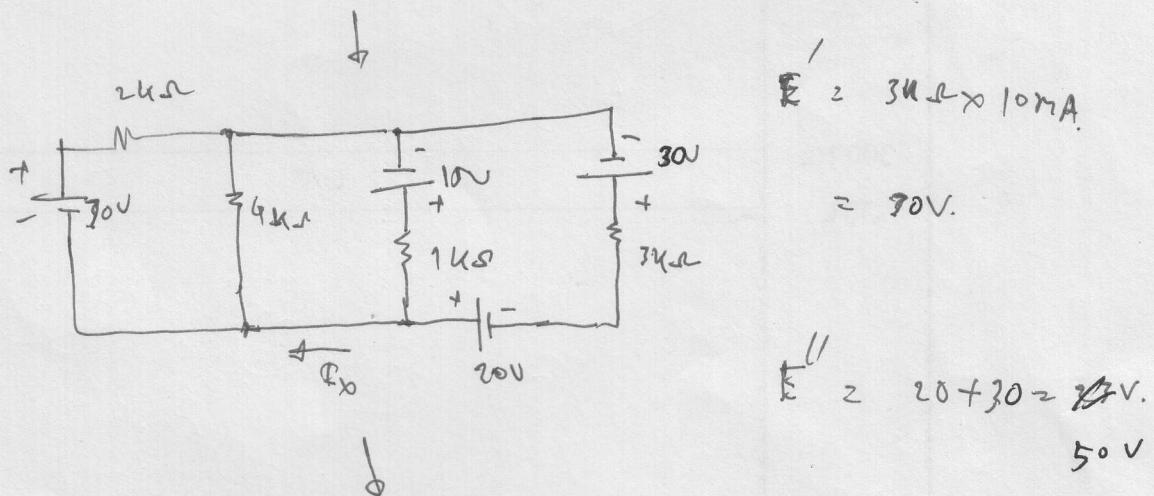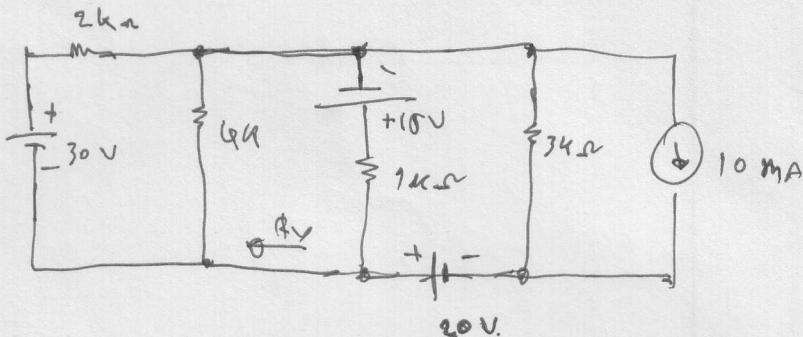zu lösen:Finden Wilson $V - \phi$
 $\phi \rightarrow V$.


$$\Phi_x' = \frac{50}{3k\Omega} V = 16.666 \text{ mA}$$

$$\Phi_{S_{02}} = 15 \text{ m} - 15 + \cancel{16.66} \text{ mA}$$

$$\Phi_{S_{02}} = \cancel{16.66} \text{ mA}$$

$$R_{T_1} = 2 \text{ k}\Omega // 4 \text{ k}\Omega = 1.333 \text{ k}\Omega$$
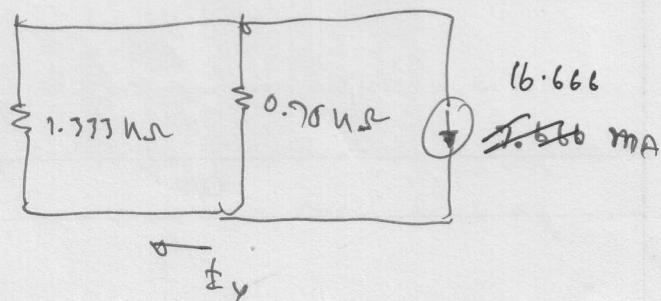
$$R_{T_2} = 1 \text{ k}\Omega // 3 \text{ k}\Omega = 0.75 \text{ k}\Omega$$




$$I_x = \frac{16.66}{\cancel{2.566} \times 0.75} = \cancel{2.566} \text{ mA} \rightarrow 6 \text{ mA}$$

$$R_H = 6 \Omega, 0W$$

41

(10) R_{Th} $\text{in } \Omega$

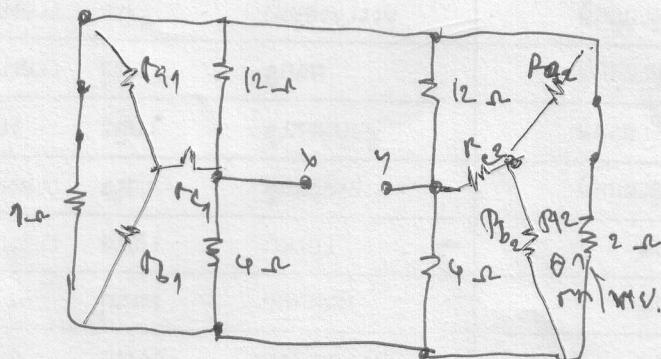

$$\begin{aligned}
 R_{T_1} &= (1+4) \parallel 12 = \frac{5 \times 12}{5+12} = \cancel{2.5 \Omega} = 3.5294 \Omega \\
 R_{T_2} &= (4+2) \parallel 12 = \frac{6 \times 12}{6+12} = 4 \Omega \\
 R_{Th} &= 4 + 3.529 = 7.529 \Omega
 \end{aligned}$$

$$R_{a_1} = \frac{1 \times 12}{1+12+4} = 0.9098 \Omega$$

$$R_{b_1} = \frac{1 \times 4}{1+12+4} = \frac{4}{17} = 0.2352 \Omega$$

$$R_{c_1} = \frac{12 \times 4}{1+12+4} = 4.827 \Omega$$

$$R_{a_2} = \frac{12 \times 2}{12+2+4} = 1.333 \Omega$$

$$R_{b_2} = \frac{2 \times 4}{12} = 0.444 \Omega$$

$$R_{C_2} = \frac{12 \times 4}{18} = 2.666$$

$$R_{T_1} = (R_{a1} + R_{a2}) // (R_{b1} + R_{b2})$$

$$= (0.9058 + 1.333) // (0.2352 + 0.444)$$

$$= \frac{(2.03) \times (0.6942)}{2.03 + 0.6942}$$

$$R_{T_1} = 0.508 \Omega$$


$$R_H = R_{C_1} + R_{T_1} + R_{C_2} = 2.823 + 0.508 + 2.666$$

$$R_H = 5.999 \Omega$$

$$R_H = 6 \Omega \quad \text{--- } \cancel{\text{H}}$$

in & 14

Tr mesh.

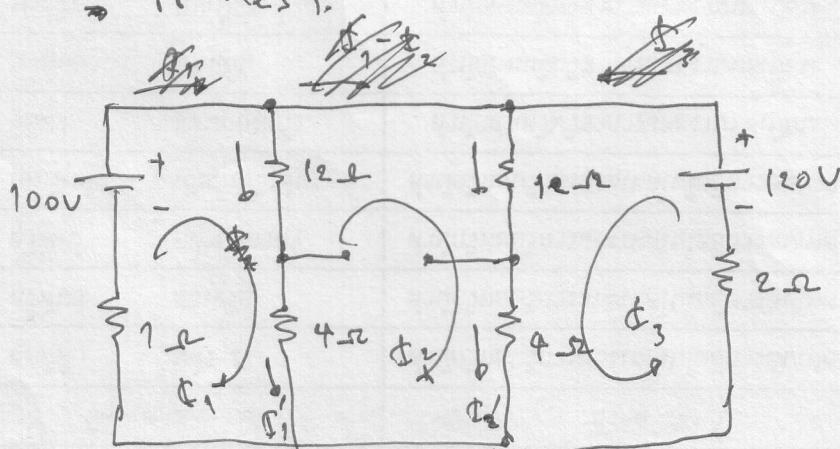

$$19f_1 - 16I_2 - 100 = 0$$


$$19f_1 - 16f_2 = 100 \quad \text{--- } ①$$

$$32I_2 - 16I_1 + 16I_3 = 0$$

$$-16I_1 + 32I_2 + 16I_3 = 0 \quad \text{---} \quad ②$$


$$18I_3 + 16I_2 - 120 = 0$$
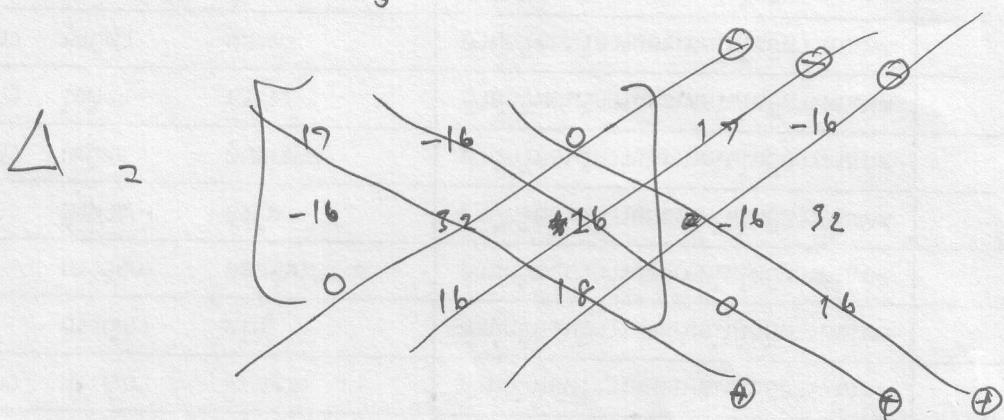
$$0 + 16I_2 + 18I_3 = 120 \quad \text{---} \quad ③$$





$$\Delta = 9792 + 0 + 0 - 0 - 4352 - 4608$$

$$\Delta = 832$$

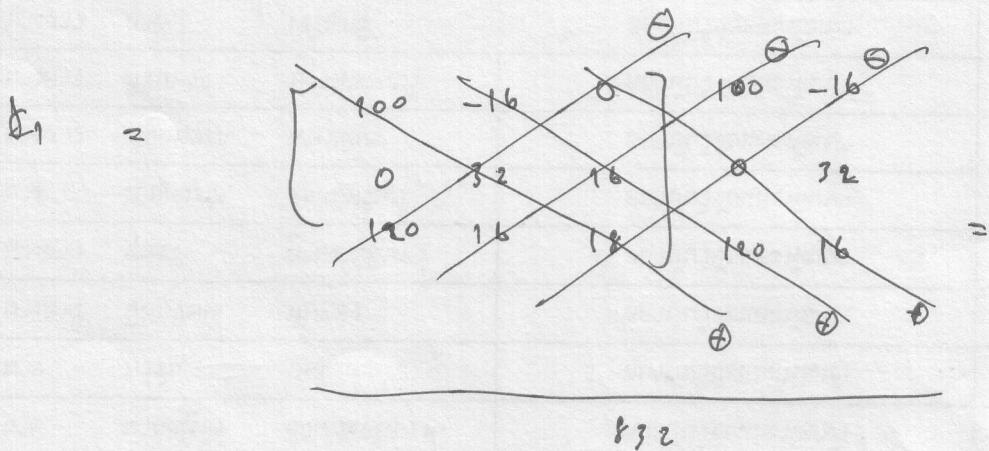

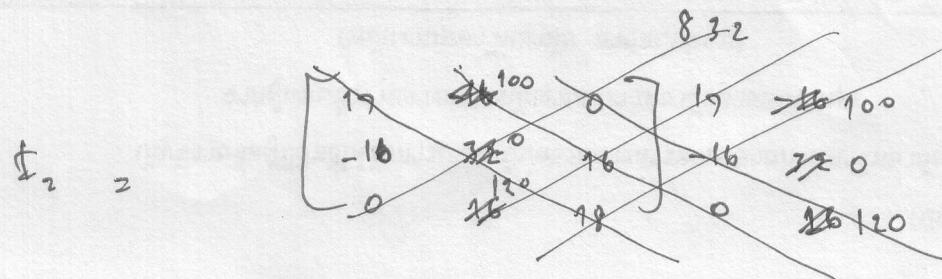
$$I_1 = \frac{57600 - 20920 + 0 - 0 - 28600 - 0}{832} = 1.538 A$$



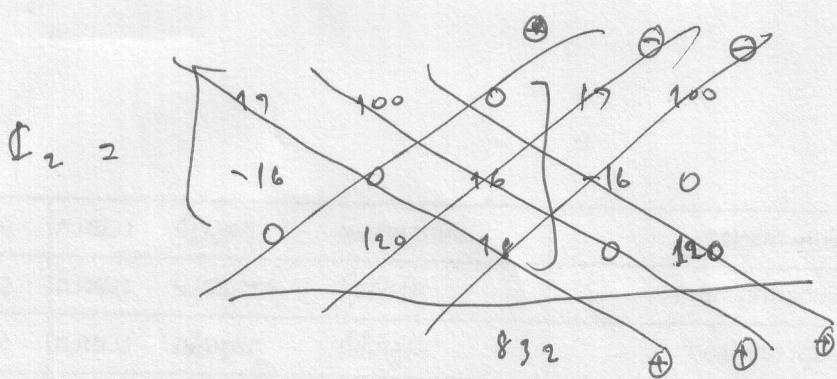

$$\Phi_2 = \frac{0 + 0 + 0 - 0 - 32,640 + 28,900}{832} = -4.6183 \text{ A}$$

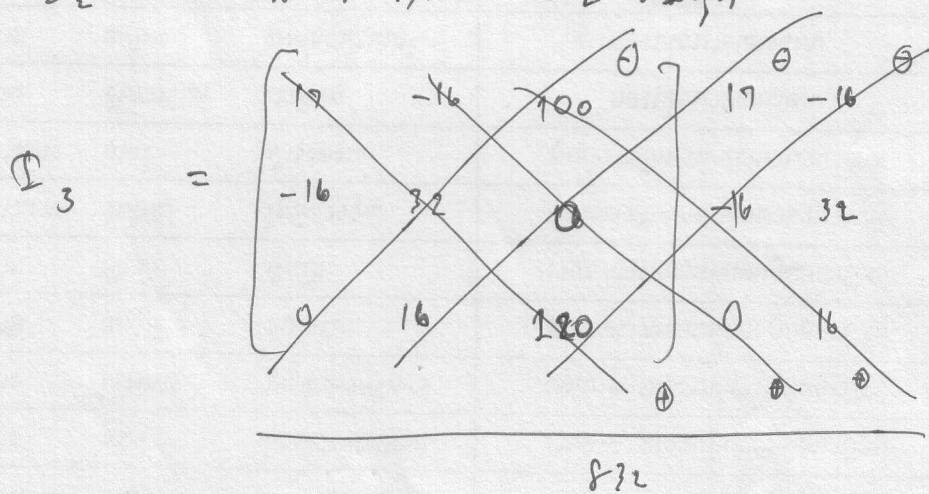Q₁ 56 5 8 d m b a r b y n n i v Q₂ B a s y o f



$$\text{C}_3 = \underbrace{68680 + 0 - 28600 - 0 - 0 - 30720}_{892}$$

$$\Phi_3 = 10.969 \text{ A}$$


$$t_1' = t_1 + t_2 = 1.538 + 4.618 = 6.1533 \text{ Å}$$

$$t_2' = t_3 - t_2 = 10.715 - 4.615 = 6.103 \text{ A}$$

$$E_{th} = (\$1 \times 4\pi) - (\$2 \times 4\pi)$$


$$E_{th} = (6.1533 \times 4\omega) - (6.1537 \times 4\omega)$$
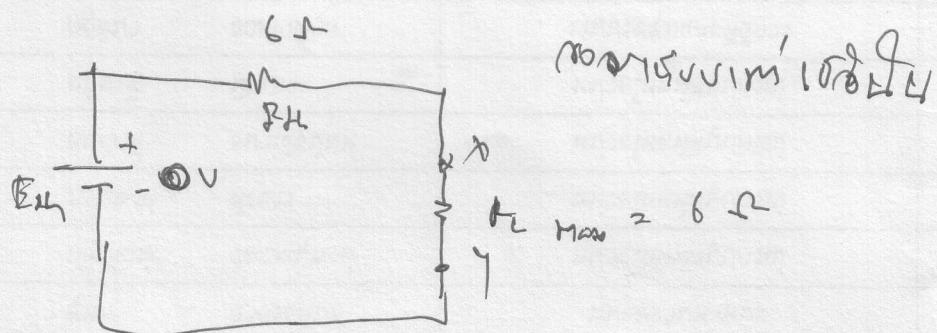
$$E_{th} = 24.614 - 24.614 = 0 \text{ V}$$



$$P_L = \frac{E_{th}^2}{4R_L} = \frac{0^2}{4 \times 6} = 0 \text{ Watt.}$$

Ans 150 mW of power in load.

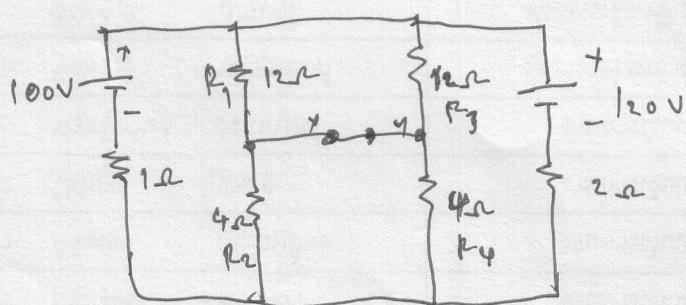


Ans 150 mW of power

$$\frac{R_1}{R_2} = \frac{R_3}{R_4} \Rightarrow \frac{12}{4} = \frac{12}{4}$$

$$\frac{R_1}{R_3} = \frac{R_2}{R_4} \Rightarrow \frac{12}{12} = \frac{4}{4}$$

Ans 150 mW of power in load.

Ans 150 mW of power in load.

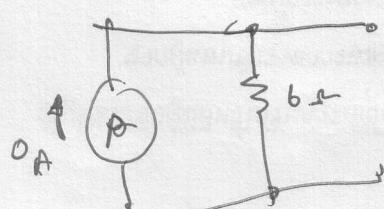

Ans 150 mW of power in load.